

ASSIGNMENT

Gajula Arun Kumar
arunkumarg099@gmail.com
IITH - Future Wireless Communications (FWC)

CONTENTS

1	Question	1
2	Components	1
3	Truth Table	1
4	Logical Diagram	1
5	K-map Implementation	1
6	Implementation	2

4 LOGICAL DIAGRAM

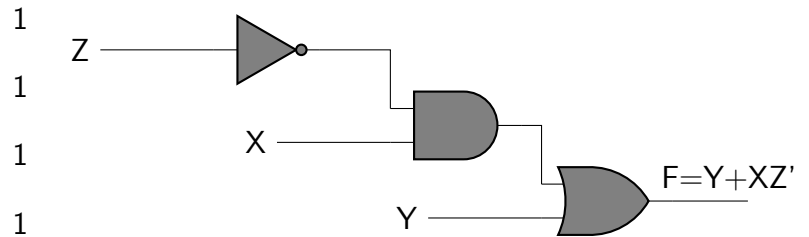


Fig. 1

1 QUESTION

A logic circuit implements the boolean function $F = X'Y + X.Y'.Z'$. It is found that the input combination $X=Y=1$ can never occur. Taking this into account, a simplified expression for F is given by

2 COMPONENTS

Component	Values	Quantity
Arduino	UNO	1
JumperWires	M-M	10
Breadboard		1
LED		2
Resistor	220ohms	1

Figure.a

3 TRUTH TABLE

X	Y	Z	F
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	X
1	1	1	X

Truth table Boolean Function "F"

5 K-MAP IMPLEMENTATION

Using the boolean logic output F can be expressed in terms of the inputs X,Y,Z with the help of the following Kmap.

		YZ			
		00	01	11	10
X	0	0	0	1	1
	1	1	0	X	X

Fig. 2

a) Reducing the boolean Function

$$F = X'Y + XY'Z'$$

$$F = X'Y(Z + Z') + XY'Z'$$

$$X'YZ + X'YZ' + XY'Z'$$

Reduced expression using K-maps is

$$F = Y + XZ'$$

6 IMPLEMENTATION

Arduino PIN	INPUT	OUTPUT
2	X	
3	Y	
4	Z	
8		F

Connections

a) Problem-1

1. Connect the circuit as per the above table.
2. Connect the output pin to LED
3. Connect inputs to Vcc for logic 1, ground for logic 0
4. Execute the circuit using the below code.

<https://github.com/aruniot099/FWC-1/blob/main/IDE/code>

b) Problem-2

1. Change the values of X,Y,Z in the code and verify the Truth Table