

ASSIGNMENT-1

Gajula Arun Kumar
arunkumarg099@gmail.com
IITH - Future Wireless Communications (FWC)

20-12-2022

Contents

- 1 Components
- 2 Truth Table
- 3 K-map Implementation
- 4 Implementation

Abstract

This manual explains about a logic circuit which implements the boolean function $F=X'Y+XY'Z'$, where the input combination $X=Y=1$ can never occur. Finding the simplified expression of F:

1 Components

Component	Values	Quantity
Arduino	UNO	1
JumperWires	M-M	10
Breadboard		1
LED		2
Resistor	220ohms	1


Figure.a

2 Truth Table

X	Y	Z	F
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	-
1	1	1	-

Truth table Boolean Function "F"

3 K-map Implementation

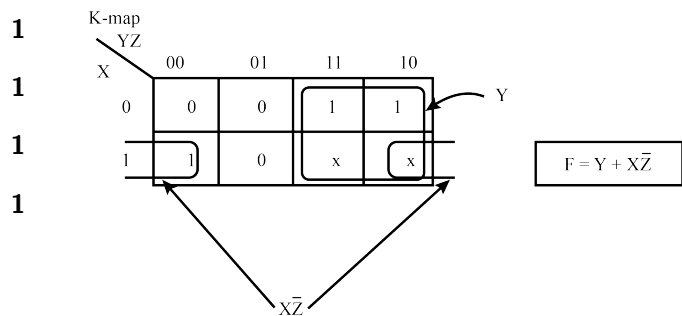

Reducing the boolean Function :

$$F=X'Y+XY'Z'$$

$$F=X'Y(Z+Z')+XY'Z'$$

$$X'YZ+X'YZ'+XY'Z'$$

Reduced expression using K-maps is

$$F=Y+XZ'$$

4 Implementation

Arduino PIN	INPUT	OUTPUT
2	X	
3	Y	
4	Z	
8		F

Connections

Problem-1 :

1. Connect the circuit as per the above table.
2. Connect the output pin to LED
3. Execute the circuit using the below code.

Problem-2 :

1. Change the values of X,Y,Z in the code and verify the Truth Table